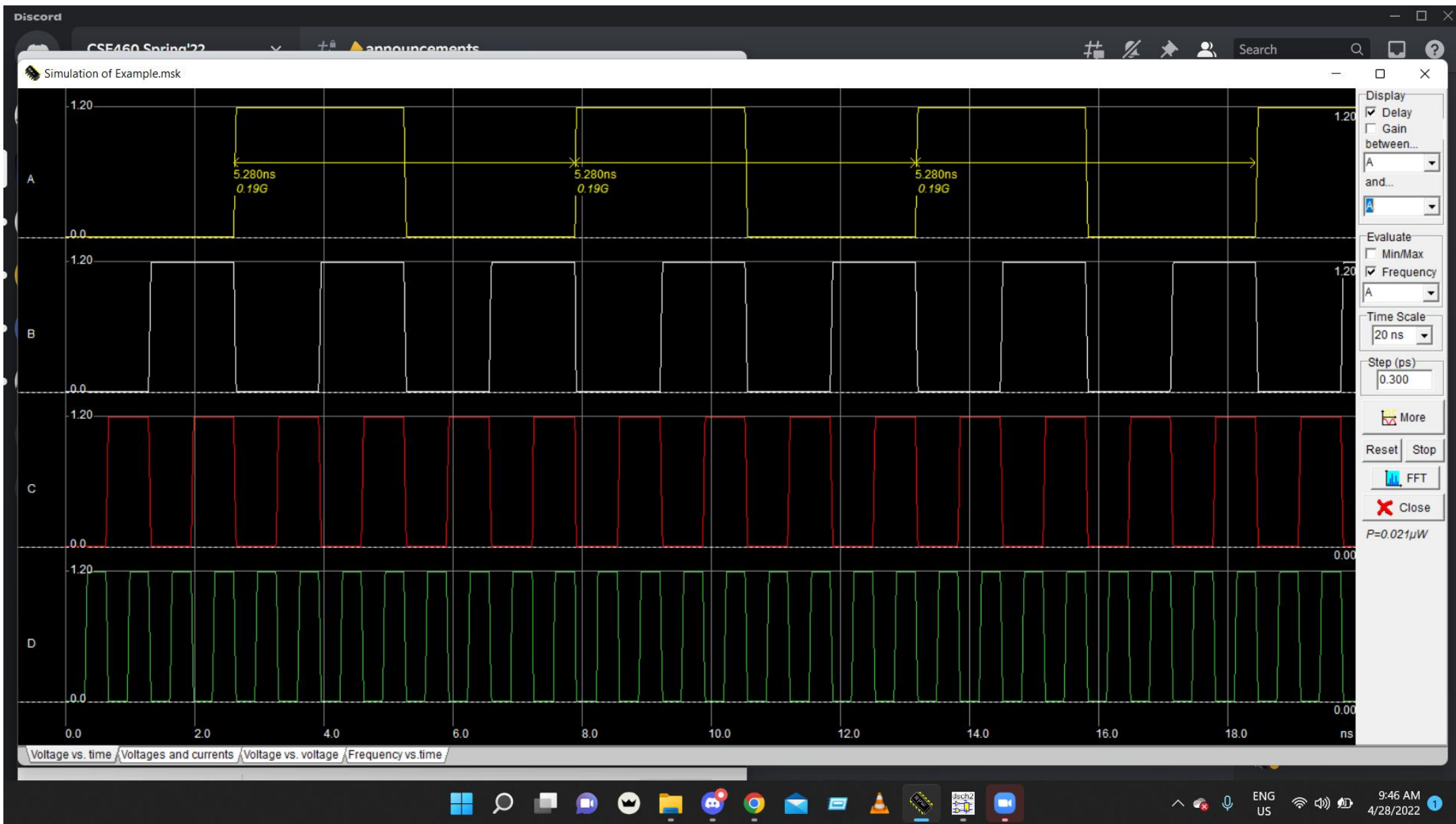


Select the area to zoom in...

CMOS 0.12um - 6 Metal (1.20V,3.30V)





Dsch2 - example

File Edit Insert View Simulate Help

Simulation Control

Fast Slow

☒ Show wire state ☐ Show pin state

Running, absolute time=320.000ns; CPU time= 4s


Circuit OK

35°C Haze

ENG US

9:33 AM 4/28/2022

Timing diagrams of example

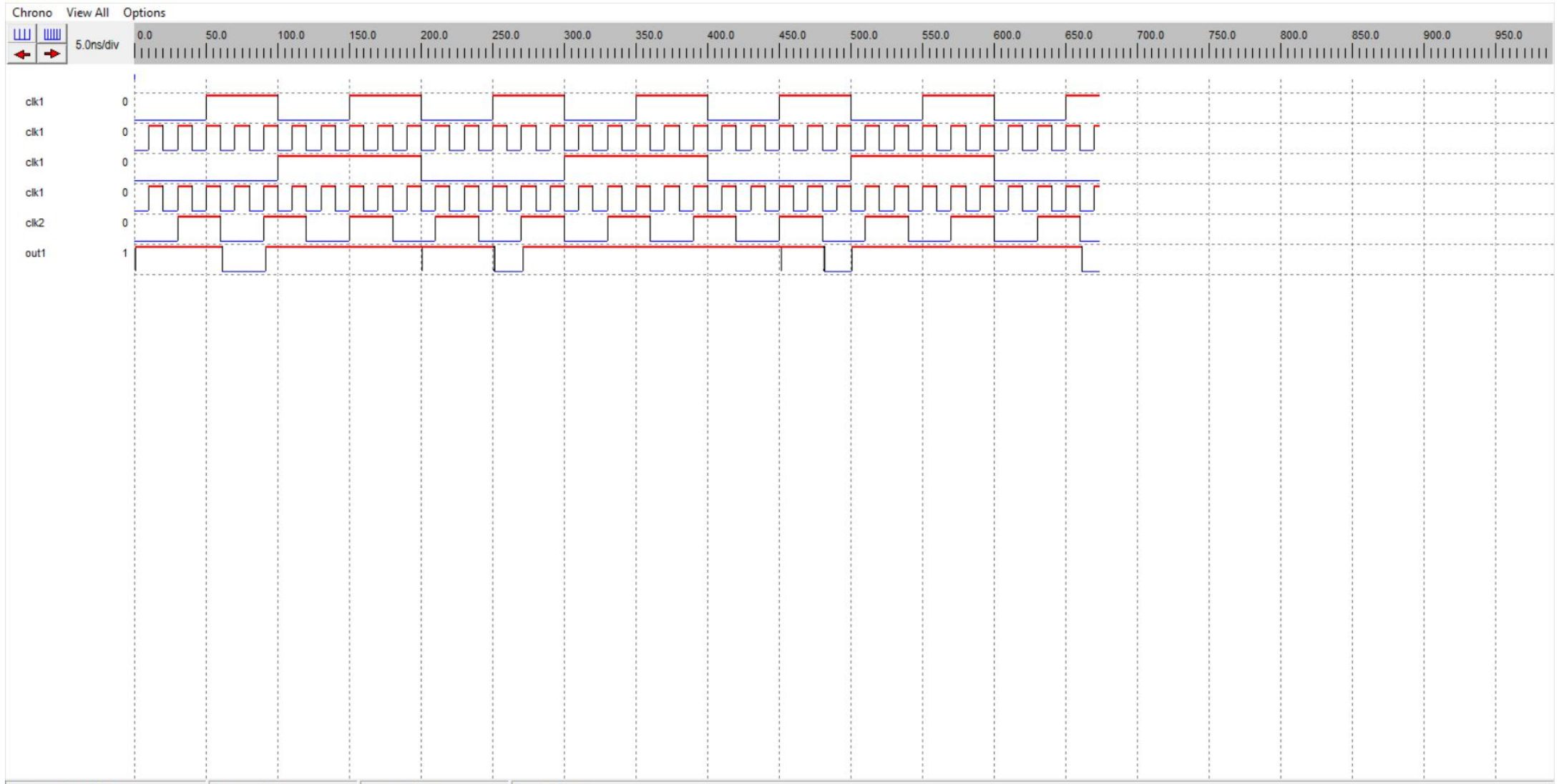

Cursor at time 626.0ns Current 1.0mA I_{max} 0.500mA Pow 0.001mW