
FARIHA RAHMAN

ID-19101038

Section 10

Lab Assignment-2

Problem 1:

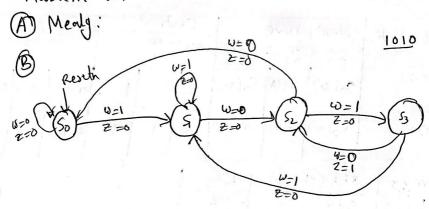

State toble

nesent	W=O V=D		0 w=1	
State	W=0	W=0	W=0	W=1
So	So	Si	0	6
Si	52	Sı	0	0
. S ₂	So	53	0	0
, 53	S2	5.2	1	0


State Assigned table


Present State	Next State V=0 V=1		w=o w=j		
00	00	01	0	G	3
0]	10	01	0	0	
10	00	11	0	0	44.7
11	(0	01	1	0	


```
module Problem1_19101038 (Clock, Resten, w, z);
input Clock, Resten, w;
output reg z;
reg [2:1]y,Y;
parameter S0=2'b00, S1=2'b01, S2=2'b10, S3=2'b11;
always @(w, y)
begin
case (y)
S0: if(w)
 begin
  Y=S1;
  z=0;
  end
  else
 begin
  Y=S0;
  z=0;
 end
S1: if(w)
 begin
  Y=S1;
  z=0;
  end
  else
 begin
  Y=S2;
  z=0;
 end
S2: if(w)
 begin
  Y=S3;
  z=0;
  end
  else
 begin
  Y=S0;
  z=0;
 end
S3: if(w)
 begin
  Y=S1;
  z=0;
  end
  else
```

```
begin
Y=S2;
z=1;
end
endcase
end
always @(negedge Resten, posedge Clock)
if (Resten==0) y<=S0;
else y<=Y;
```

endmodule

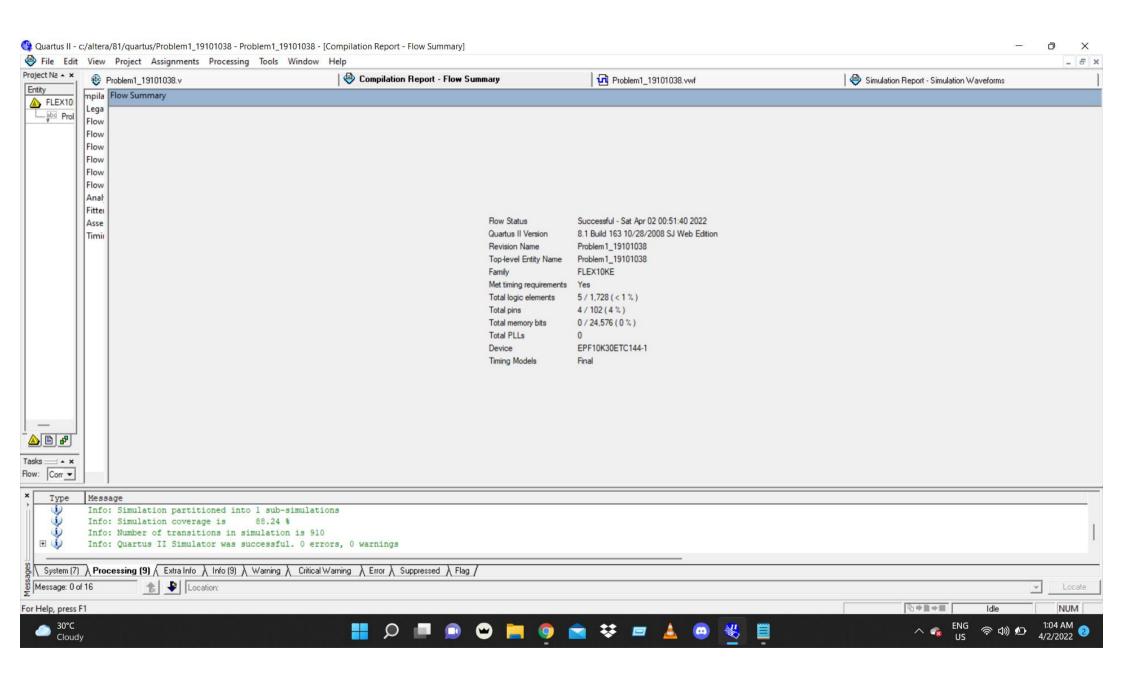

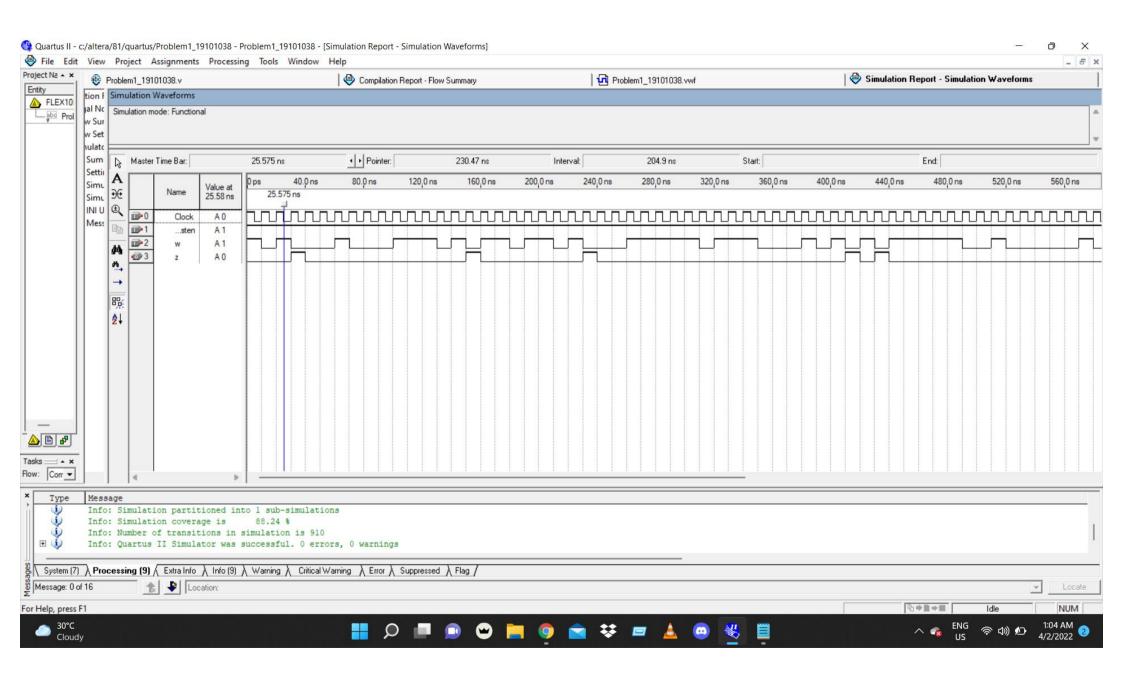

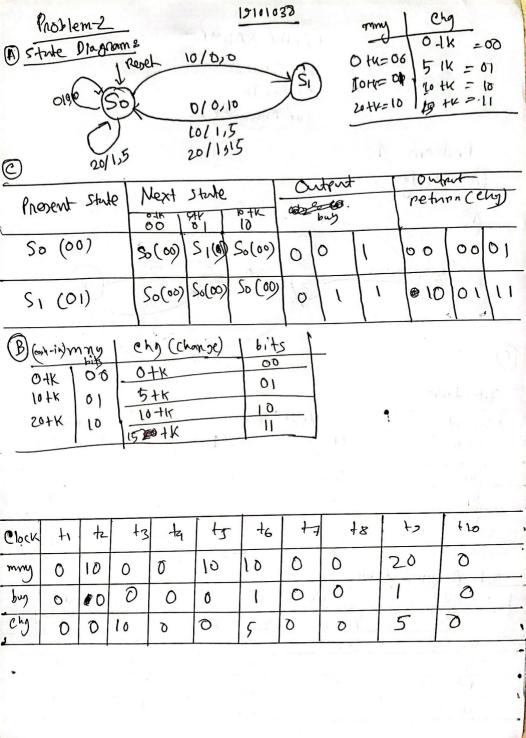

```
module Problem2 19101038(clock, reset, mny, buy, present state, next state, chg);
input clock, reset;
input [1:0] mny;
output reg buy; // output z = 1 or 0
output reg [1:0] chg, present state, next state;
parameter state0tk= 2'b00, // 0tk/final state
  state10tk= 2'b10, // 10tk state
  product = 15; // what I am buying, 10/15/20 tk profuct
always@(posedge clock)
begin
 begin
 if(reset==1)
 begin
  present state=0;
  next state=0;
  end
  else
 begin
  present state=next state;
  case(present state)
  state0tk: if(mny == 2'b00) // 0 tk
    begin
    next state = state0tk;
    buy =0;
     chg = 2'b00;
    end
   else if(mny == 2'b01) // 10 \text{ tk}
    begin
    next state=state10tk;
     buy=0;
     chg=2'b00;
    end
   else if(mny == 2'b10) // 20 tk
    begin
    next state = state0tk;
    buy = 1;
     chg = 2'b01;
    end
  state 10tk: if(mny == 2'b00)
    begin
    next state = state0tk;
     buy =0;
     chg = 2'b10;
    end
   else if(mny == 2'b01)
    begin
    next state=state0tk;
     buy= 1;
     chg = 2'b01;
    end
   else if(mny == 2'b10)
    begin
```

```
next_state=state0tk;
buy=1;
chg=2'b11;
end

endcase
end
end
end
end
end
endmodule
```

